

# Tutorial 4 Questions

Nan Meng


University of Hong Kong

*u3003637@connect.hku.hk*

February 29, 2016

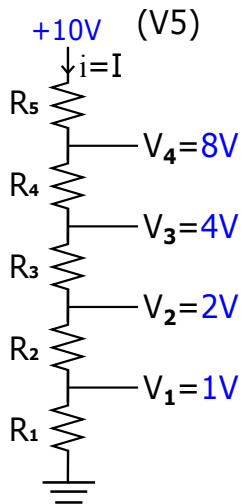
## Question 1

- \* Determine the resistance value of  $R_1, R_2, \dots, R_5$  in the circuits. (Assume the resistance of  $R_1$  is  $R$ )



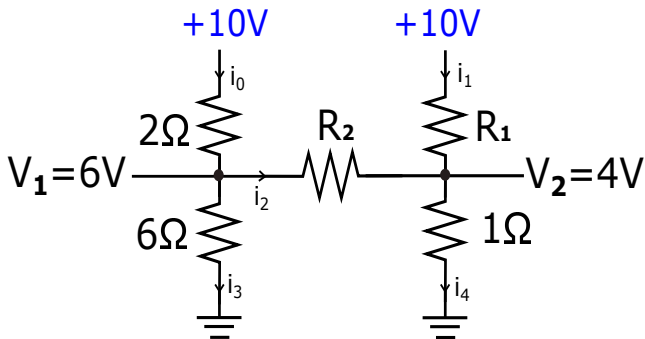
## Question 2

- \* Determine the resistance of  $R_1$  and  $R_2$  in the circuit.



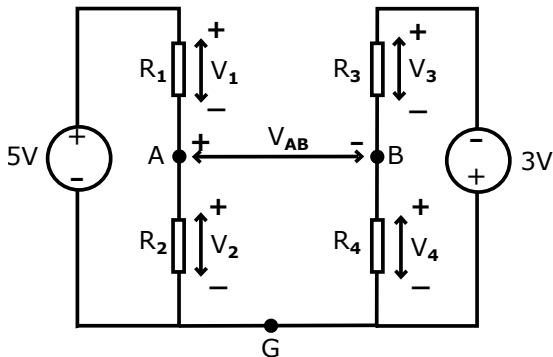
## Question 3

- If  $V_{AB} = 4V$ , determine  $R_1, R_2, R_3$  and  $R_4$ .



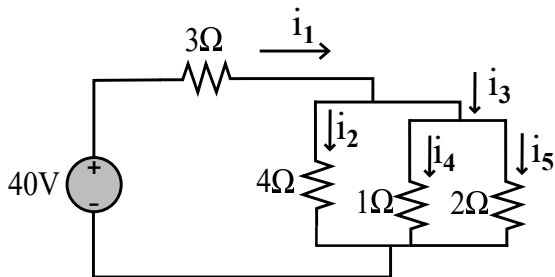
## Question 4

- For the circuit in the figure, determine  $i_1$  to  $i_5$ .




## Question 5

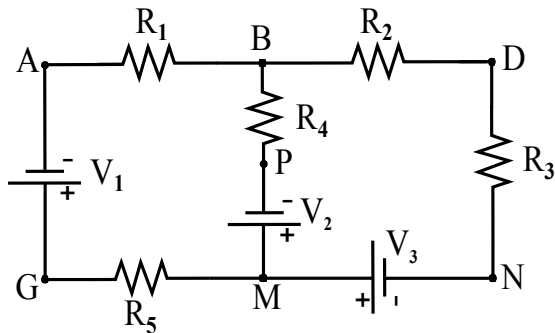

- \*  $R_1 = 80\Omega, R_2 = 10\Omega, R_3 = 20\Omega, R_4 = 90\Omega, R_5 = 100\Omega$
- \* Battery:  $V_1 = 12V, V_2 = 24V, V_3 = 36V$
- \* Resistor:  $I_1, I_2, \dots, I_5 = ?$        $P_1, P_2, P_5 = ?$
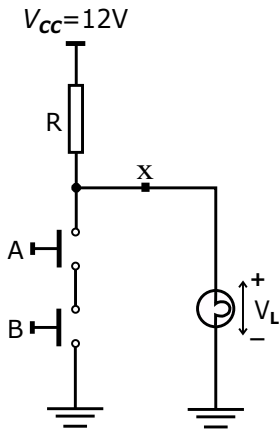
## Question 6


- \* You have connected the lamp, with  $V_{CC} = 12V$ . The datasheet of the lamp states that it only turns on when  $V_L > 8V$ . The lamp has an internal resistance of  $1k\Omega$ .
- \* What is the range of  $R$  that would allow the circuit to function correctly with all input combinations.



## Question 7a

- \* A force sensitive resistor (FSR) is a resistor with its resistance changed according to the force applied to it.
- \* For simplicity sake, your partner has wired up the FSR using a simple potential divider circuit


Force (N)	Resistance $R_{fsr}(\Omega)$
0	<b>1M</b>
0.5	<b>10k</b>
1	<b>6k</b>
10	<b>1k</b>

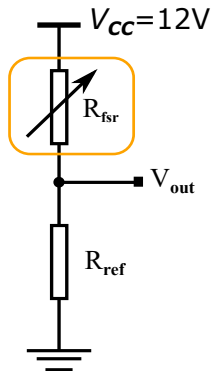


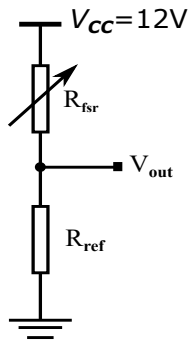
## Question 7a

- \* Calculate the following quantities when  $R_{ref} = 10k\Omega$ :
  - Voltage across the FSR;
  - Voltage at  $V_{out}$ ;
  - Current owing through the FSR.




## Question 7b

- \* The output  $V_{out}$  is used to detect the presence of a ball. Due to its light weight, the ball produces only 0.5N when it is located on top of the sensor. The rest of the system requires that  $V_{IL} = 2V$  and  $V_{IH} = 10V$ 
  - $V_{IL}$ : Max. voltage that the system regards as logical LOW
  - $V_{IH}$ : Min. voltage that the system regards as logical HIGH
- \* Determine the range of value that  $R_{ref}$  may take for correct functioning of the circuit.
  - It should output a logical HIGH when a ball is presence and a logical LOW otherwise.
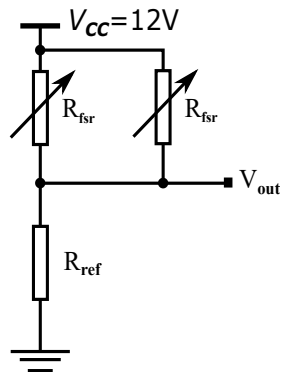
## Question 7c


- \* Your partner suggests that it may be possible to use 2 FSRs connected to perform a logical OR operation: When the ball rolls over either one of the 2 FSRs, the output  $V_{out}$  is HIGH, and is LOW otherwise.

- \* What is the output voltage  $V_{out}$ ?
  - one of the FSRs is under pressure of 0.5N;
  - both FSRs are under a pressure of 0.5N each;
  - none of the FSRs is under pressure;
  - assume  $R_{ref}$  is  $100k\Omega$


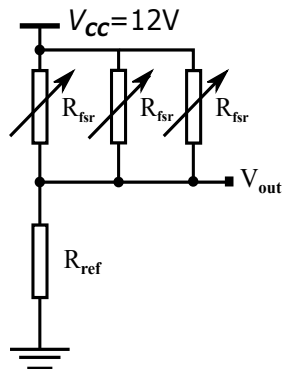
## Question 7d

- \* Recall that  $V_{IL}$  is 2V and  $V_{IH}$  is 10V, is the circuit functioning correctly as a 2-input OR?
- \* If there are 3 FSRs connected in parallel, assumer  $R_{ref}$  remains at 100k, will the circuit behave as a 3-input OR?




## Appendix(Question 8)

\* Find  $V_2$  using single loop analysis


- Without simplifying the circuit
- Simplifying the circuit
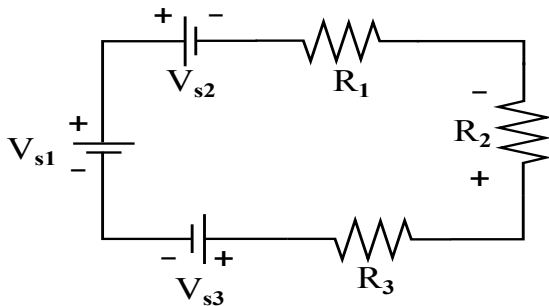
$$V_{s1} = 2V, V_{s2} = 2V, V_{s3} = 2V, R_1 = 1\Omega, R_2 = 2\Omega, R_3 = 4\Omega$$



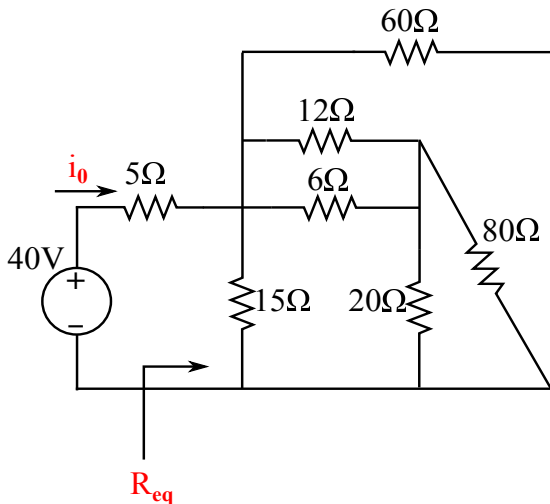
## Appendix(Question 9)

- \* Find  $R_{eq}$  and  $i_o$  in the circuit of the figure.


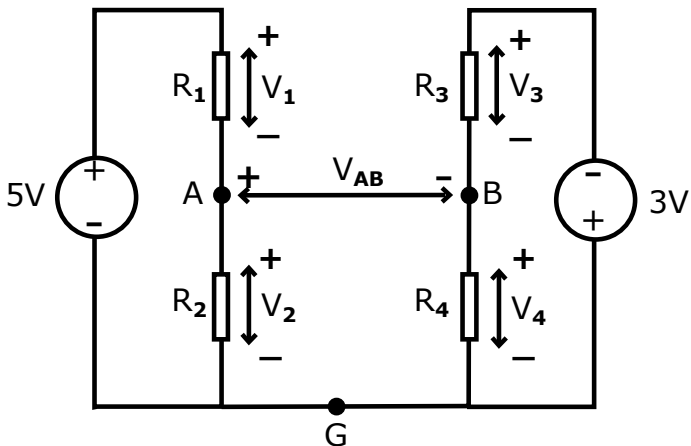
## Appendix(Question 10)

Assume all resistors have the same resistance,  $R$ . Determine the voltage  $V_{AB}$ .



# Appendix(Rules Governing Currents and Voltages)

## Rule 1: Currents flow in loops

The same amount of current flows into the bulb (top path) and out of the bulb (bottom path)

## Rule 2: Like the flow of water, the flow of electrical current (charged particles) is incompressible

Kirchoffs Current Law (KCL): the sum of the currents into a node is zero

## Rule 3: Voltages accumulate in loops

Kirchoffs Voltage Law (KVL): the sum of the voltages around a closed loop is zero




## Appendix(Analyzing Circuits)

- Assign **node voltage variables** to every node except ground (whose voltage is arbitrarily taken as zero)
- Assign **component current variables** to every component in the circuit
- Write one **constructive relation** for each component in terms of the component current variable and the component voltage
- Express **KCL** at each node except ground in terms of the component currents
- **Solve** the resulting equations
- $Power = IV = I^2R = V^2/R$


## Appendix(Parallel/Series Combinations of Resistance)

- To simplify the circuit for analysis

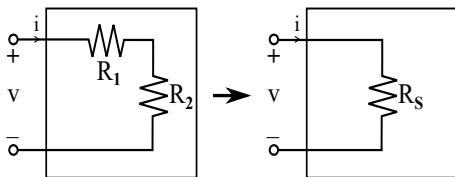

$$\begin{aligned}v &= R_1 i + R_2 i \\v &= R_s i \\ \therefore R_s &= R_1 + R_2\end{aligned}$$


**Series**

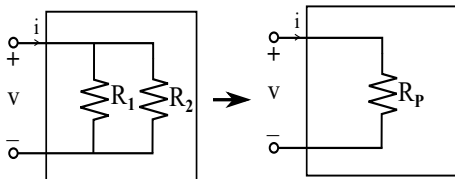

$$\begin{aligned}R_p &= \frac{1}{1/R_1 + 1/R_2} = \frac{R_1 R_2}{R_1 + R_2} \\ &= R_1 \parallel R_2\end{aligned}$$


**Parallel**

## Appendix(Voltage/Current Divider)

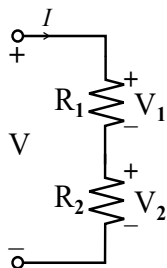

← **Voltage Divider**
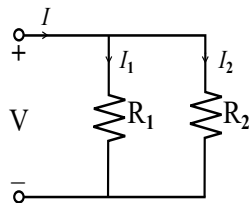
$$I = \frac{V}{R_1 + R_2}$$
$$V_1 = R_1 I = \frac{R_1}{R_1 + R_2} V$$
$$V_2 = R_2 I = \frac{R_2}{R_1 + R_2} V$$



**Current Divider** →

$$V = (R_1 \parallel R_2) I$$
$$I_1 = \frac{V}{R_1} = \frac{R_1 \parallel R_2}{R_1} I = \frac{R_2}{R_1 + R_2} I$$
$$I_2 = \frac{R_1}{R_1 + R_2} I$$

# The End